

Ohm's Law Assignment 1

You will calculate the amount of resistance needed to complete the following circuit using the following link:

<http://tinyurl.com/y9fk2v7j>

You will post the link of the completed diagram on a word document with the required resistance.

- Battery: 9V
- LED Details: 2V and 15mA
- R = _____
- Diagram Link: